

# 计算机设计与实践

——CPU 设计实验报告

学号：1130310128

学院：计算机科学与技术学院

姓名：杨尚斌

指导老师：罗丹彦

# 实验目的

- 1. 掌握 Xilinx ISE 集成开发环境和 ModelSIM 仿真工具的使用方法。
- 2. 掌握 VHDL 语言。
- 3. 掌握 FPGA 编程方法及硬件调试手段。
- 4. 深刻理解处理器结构和计算机系统整体工作原理。

# 实验环境

## 开发软件

Xilinx ISE 9.1

ModelSIM 6.5

## 开发板

COP2000+实验台

# 实验设计

## CPU 接口信息定义

信号名	位数	方向	来源/去向	意义
RST	1	in	外部复位信号	系统复位使能端
CLK	1	in	外部时钟	系统时钟
ABUS	16	out	存储器	地址总线
DBUS	16	inout	存储器	数据总线
nMREQ	1	out	存储器	存储器片选
nRD	1	out	存储器	存储器读
nWR	1	out	存储器	存储器写
nBHE	1	out	存储器	存储器高位有效
nBLE	1	out	存储器	存储器低位有效

# CPU 设计方案

## 1. 指令格式设计

指令由操作码和地址码两部分组成，在指令系统中所有的指令都是二进制指令。

通用寄存器有 8 个，所以需要 3 为地址与之对应。

访存的时候形式地址为 8 位。

定义指令的高 5 位为操作码。

因此，做下面的定义：

OP (5)	AD1 (3)		AD2 (3)
--------	---------	--	---------

(寄存器-寄存器型指令)

OP (5)	AD1 (3)	AD2 (8)
--------	---------	---------

(其他类型指令)

## 2. 微操作定义

指令名称	助记符	二进制操作码
加法操作	ADD	00000
减法操作	SUB	00001
寄存器传送	MOV	00010
立即数传送	MVI	10010
取数操作	LDA	11011
存数操作	STA	11000
无条件跳转操作	JMP	10001
条件跳转	JZ	10000


JMP X	15	11	10	8	7	0
	00000	000	X			
	R7//X → PC					
JZ Ri, X	15	11	10	8	7	0
	00010	Ri	X			
	if Ri=0 then R7//X → PC					
SUB Ri, Rj	15	11	10	8	7	3 2 0
	00100	Ri	00000	Rj		
	Ri-Rj → Ri					
ADD Ri, Rj	15	11	10	8	7	3 2 0
	00110	Ri	00000	Rj		
	Ri+Rj → Ri					
MVI Ri, X	15	11	10	8	7	0
	01000	Ri	X			
	X → Ri					
MOV Ri, Rj	15	11	10	8	7	3 2 0
	01010	Ri	00000	Rj		
	Rj → Ri					
STA Ri, X	15	11	10	8	7	0
	01100	Ri	X			
	Ri → R7//X					
LDA Ri, X	15	11	10	8	7	0
	01110	Ri	X			
	R7//X → Ri					

### 3. 节拍划分

共有 5 个节拍：

T0	取指
T1	PC+1
T2	运算器模块
T3	存储器模块
T4	回写

### 4. 处理器结构设计框图和功能描述

 

## 5. 各模块结构信号定义

### a) 节拍计数器

**模块说明：**此模块为时钟模块，是一个 5 节拍的计数器。当 `clk` 信号产生一个脉冲的时候，`t` 就会循环的改变第 `i` 位的值，最后达到节拍的效果。

**接口说明：**

信号名	位数	方向	来源/去向	意义
<code>clk</code>	1	in	系统时钟	外接系统时钟
<code>reset</code>	1	in	系统复位	外接系统复位
<code>t</code>	5	out	各模块节拍	对外输出节拍（5 节拍）

## b) 取指模块

**模块说明：**此模块为取指模块，负责取指令阶段，并且在取到指令之后对其他模块发出取到的指令 IR 和地址 PC，除此之外还接收回写模块发出的 pcupdate 和 pcnew 指令，用来回写 pc。此模块分为两个节拍进行，在  $t_0 = 1$  的时候完成取指和 pc 的回写，在  $t_1 = 1$  的时候完成  $pc+1$  的操作。

**接口说明：**

信号名	位数	方向	来源/去向	意义
lrnew:	16	In	访存控制 IR	接受从存储器中读取的新指令。
pcnew:	16	in	回写模块 PCnew	接受从回写模块发出的 pc 复写值。
clk:	1	In	系统时钟	接受系统时钟。
pcupdate:	1	In	回写模块 Pcupdate	pc 复写使能端。
reset:	1	In	系统复位	接受复位信号，置 $pc=0$ 。
t0、t1:	1	In	时钟模块 t	节拍信号。
irout:	16	Out	各模块 ir	对外输出指令 ir。
pcout:	16	Out	访存控制 PCout、回写模块 PCin	对外输出 pc 值。
irreq:	1	Out	访存控制 irreq	发出读取 ir 的使能信号。

## c) 运算模块

**模块说明：**此模块为运算器模块 ALU，负责各种计算任务。当回写使能信号 enable\_wb 为 1 的时候，寄存器 ir 按照回写模块传送过来的 reg\_wb 进行更新。当 enable\_t( $t(2)$ )有效的时候，开始运行计算任务，并且把最后计算得出的值传给 sig\_reg7aluout，如果计算内容和地址有关系，则传 R7 与地址并起来给访存控制模块。

接口说明：

信号名	位数	方向	来源/去向	意义
<b>enable_t</b>	<b>1</b>	<b>In</b>	<b>时钟模块</b>	<b>驱动当前模块</b>
Ir	16	In	取指模块	判断当前的运算方法以及需要的值
Sig_reg7aluout	16	Out	访存控制模块和存储模块	暂时寄存器
Sig_reg7addrout	16	Out	访存控制模块	和 R7 并在一起，输入至访存控制模块
Enable_tb	1	In	回写模块	回写寄存器使能信号
Reg_wb	8	In	回写模块	要回写的寄存器的值

#### d) 存储模块

**模块说明：**此模块为存储管理模块，主要负责运算模块输出的值和取数时访存控制的值，用来向回写模块提供寄存器要回写的值，在  $t_3 = 1$  的时候进行驱动。

接口说明：

信号名	位数	方向	来源/去向	意义
Aluout	7	In	运算模块的 Sig_reg7aluout，取低八位	接收 alu 传来的值。
IR	16	In	取指模块	接收取指模块传出的 ir。
Data	8	In	访存控制	接收取数时访存控制中的数据。
T	1	In	时钟模块 t	接收节拍。
Rtemp	8	Out	回写模块 Rtemp	对回写模块输出要回写的数值
nMRD	1	Out	访存控制模块	读标志
nMWR	1	Out	访存控制模块	写标志

e) 回写模块

模块说明：此模块为回写模块，主要用来对 Pc 和寄存器进行回写，当  $t_4 = 1$  的时候开始执行。顺便对 JZ 操作在这里进行相关的判断。

信号说明：

信号名	位数	方向	来源/去向	意义
PCin	16	In	取指模块	接收取指模块传来的 PC
T	1	In	时钟模块	节拍控制
Rtemp	8	In	存储模块	接收存储模块的寄存器的值
Cy	1	In	运算模块	接收 ALU 传来的进位
Rupdate	1	Out	运算模块	更新寄存器使能信号
Rdata	8	Out	运算模块	寄存器要更新的值
PCupdate	1	Out	取指模块	Pc 更新使能信号
PCnew	16	Out	取指模块	PC 要更新的值

f) 访存控制模块

模块说明：此模块为访存控制模块，是 CPU 设计的核心模块。主要设计三部分，取指，取数，存数，分别由 irrep, nMRD, nMWR 驱动。当 Irrep = 1 时, 主存片选有效，对主存 ABUS 输出地址，IR 得到 DBUS 的数据； 当 nMRD = 0 时，开始进行读数操作，主存片选有效，ABUS 输出地址，data 输出 DBUS 的低 8 位值；当 nMWR = 0 时，开始写数才做，主存片选有效，主存 ABUS 输出地址，DBUS 输出要写入的值。

信号说明：

信号名	位数	方向	来源/去向	意义
IRreq	1	In	取指模块	IR 使能
IR	16	Out	取指模块	对取指模块输出 IR
PCout	16	In	取指模块	接收取指指令
ALUOUT	8	In	运算模块	写数时使用



Addr	16	In	运算模块	读数时使用
ABUS	16	Out	主存储器	对主存输出地址
DBUS	16	Inout	主存储器	数据总线
nWR	1	Out	主存储器	写主存使能信号
nRD	1	Out	主存储器	读主存使能信号
nMREQ	1	Out	主存储器	片选信号
NBHE	1	Out	主存储器	高字节允许访问
nBLE	1	Out	主存储器	低字节允许访问
nMWR	1	In	存储模块	写数使能
nWRD	1	In	存储模块	读数使能
Data	8	Out	存储模块	对存储模块输出取到的数据

## g) 总体设计

信号说明：

信号名	位数	方向	来源/去向	意义
RST	1	in	外部复位信号	系统复位使能端
CLK	1	in	外部时钟	系统时钟
ABUS	16	out	存储器	地址总线
DBUS	16	inout	存储器	数据总线
nMREQ	1	out	存储器	存储器片选
nRD	1	out	存储器	存储器读
nWR	1	out	存储器	存储器写
nBHE	1	out	存储器	存储器高位有效
nBLE	1	out	存储器	存储器低位有效

元件例化代码：

```

signal t : STD_LOGIC_VECTOR(4 downto 0);      --正常节拍
signal IR_C_F : STD_LOGIC_VECTOR(15 downto 0); -- 取指模块取出的 ir
signal PCout_F_CW : STD_LOGIC_VECTOR(15 downto 0); -- PC 送往访存控制取指，送回写模块
signal PCnew_W_F : STD_LOGIC_VECTOR(15 downto 0); -- 跳转的时候要更新的 PC
signal PCupdate_W_F : STD_LOGIC;              -- 跳转更新 PC 使能信号
signal irout_F_ASW : STD_LOGIC_VECTOR(15 downto 0); --取指模块取到的 Ir,会送往
ALU 存储 和回写

```

```

signal irreq_F_C : STD_LOGIC;          -- 取指送往访存控制，告诉要取指令了
signal ALUOUT_A_CS : STD_LOGIC_VECTOR(15 downto 0);  ---ALU 送往其他模块的 aluout
signal Addr_A_C : STD_LOGIC_VECTOR(15 downto 0);    --- ALU 送往访存的 addr
signal Rupdate_W_A : STD_LOGIC;                    ---回写模块送往 ALU 的更改寄存器使能信号
signal Rdata_W_A : STD_LOGIC_VECTOR(7 downto 0);    ----回写模块输出的要更新的寄存器的值
signal data_C_S : STD_LOGIC_VECTOR(7 downto 0);    -- 取数的时候使用
signal nMWR_S_C : STD_LOGIC;                       --写数使能
signal nMRD_S_C : STD_LOGIC;                       --读数使能
signal Rtemp_S_W : STD_LOGIC_VECTOR(7 downto 0);   -- 存储模块向回写模块
signal cy_A_W : STD_LOGIC;                         --进位

    u1: clock port map(CLK, RST, t);
    u2: fetch port map(IR_C_F, PCnew_W_F, CLK , PCupdate_W_F, RST, t(0), t(1),
irout_F_ASW, PCout_F_CW, irreq_F_C);
    u3: ALU port map(t(2), irout_F_ASW, ALUOUT_A_CS, Addr_A_C, Rupdate_W_A,
Rdata_W_A, cy_A_W);
    u4: control port map(irreq_F_C, IR_C_F, PCout_F_CW, ALUOUT_A_CS(7 downto 0),
Addr_A_C, ABUS, DBUS, nWR, nRD, nMREQ, nBHE, nBLE, nMWR_S_C, nMRD_S_C ,
data_C_S);
    u5: save port map(t(3), ALUOUT_A_CS(7 downto 0), data_C_S, nMWR_S_C,
irout_F_ASW, nMRD_S_C, Rtemp_S_W);
    u6: write_back port map(PCout_F_CW, t(4), Rtemp_S_W, irout_F_ASW, cy_A_W,
Rupdate_W_A, Rdata_W_A, PCupdate_W_F, PCnew_W_F);

```

## 6. 波形仿真

### a) 节拍计数器

核心代码：

```

entity clock is
    Port ( clk : in  STD_LOGIC;
          reset : in  STD_LOGIC;
          t : out  STD_LOGIC_VECTOR (4 downto 0));
end clock;
process(clk, reset)
    variable tep : integer range 0 to 6 := 0;
begin


```

```

if(reset = '1') then
    t <= "00000";
    tep := 0;
elsif (clk = '1' and clk' event) then
    tep := tep + 1;
    if tep = 6 then
        tep := 1;
    end if;
    case tep is
        when 1 => t <= "00001";
        when 2 => t <= "00010";
        when 3 => t <= "00100";
        when 4 => t <= "01000";
        when 5 => t <= "10000";
        when others => NULL;
    end case;
end if;
end process;

```

仿真波形:

 

## b) 取指模块

核心代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```




entity fetch is
    Port ( irnew : in  STD_LOGIC_VECTOR (15 downto 0);           --访存模块输入的
    IR
    pcnew : in  STD_LOGIC_VECTOR (15 downto 0);                 --回写模块,
    更新 PC
    clk : in  STD_LOGIC;                                         --节拍
    pcupdate : in  STD_LOGIC;                                    --告诉要更新
    PC 了
    reset : in  STD_LOGIC;                                       --复位
    t0 : in  STD_LOGIC;
    t1 : in  STD_LOGIC;
    irout : out  STD_LOGIC_VECTOR (15 downto 0);                --输出的 IR
    pcout : out  STD_LOGIC_VECTOR (15 downto 0);
    irrep : out  STD_LOGIC;                                     --使能

end fetch;

architecture Behavioral of fetch is
    signal pc : STD_LOGIC_VECTOR (15 downto 0);
    begin
        process(clk, reset, t0, t1, pcupdate)
        begin
            if reset = '1' then
                irrep <= '0';
                pc <= "0000000000000000";
            elsif t0 = '1' then
                irrep <= '1';
                irout <= irnew;
            elsif t1 = '1' then
                irrep <= '0';
                if (clk = '1' and clk' event) then
                    pc <= pc + 1;
                end if;
            elsif pcupdate = '1' then
                pc <= pcnew;
                irrep <= '0';
            end if;
            pcout <= pc;
        end process;
    end Behavioral;
end

```

仿真波形:

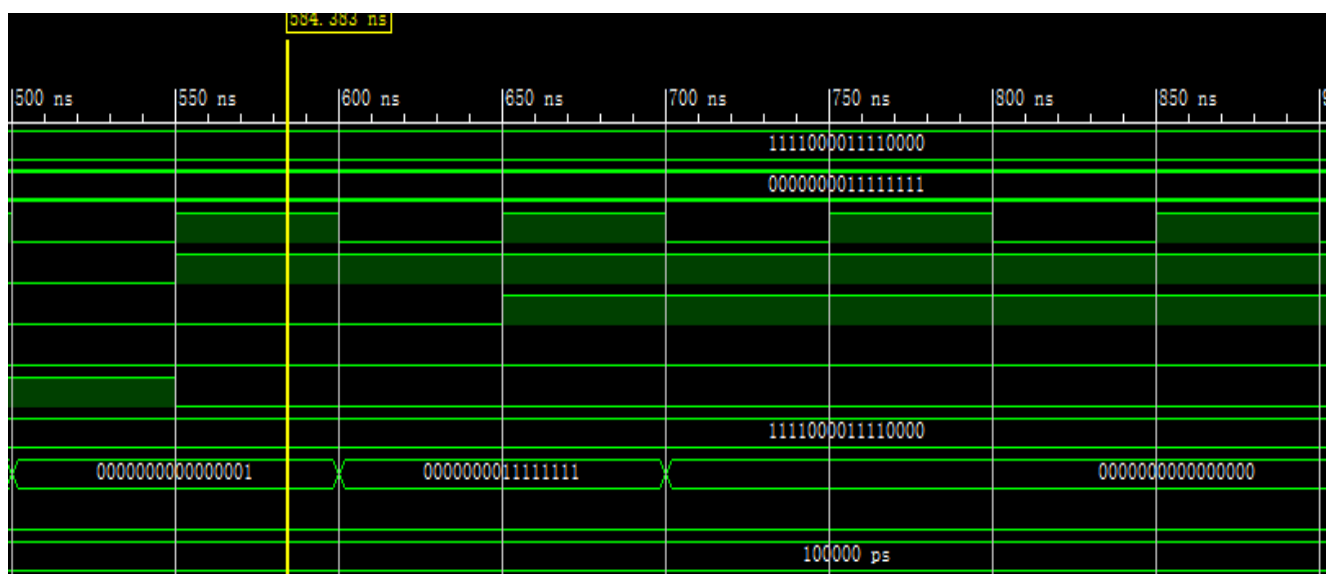 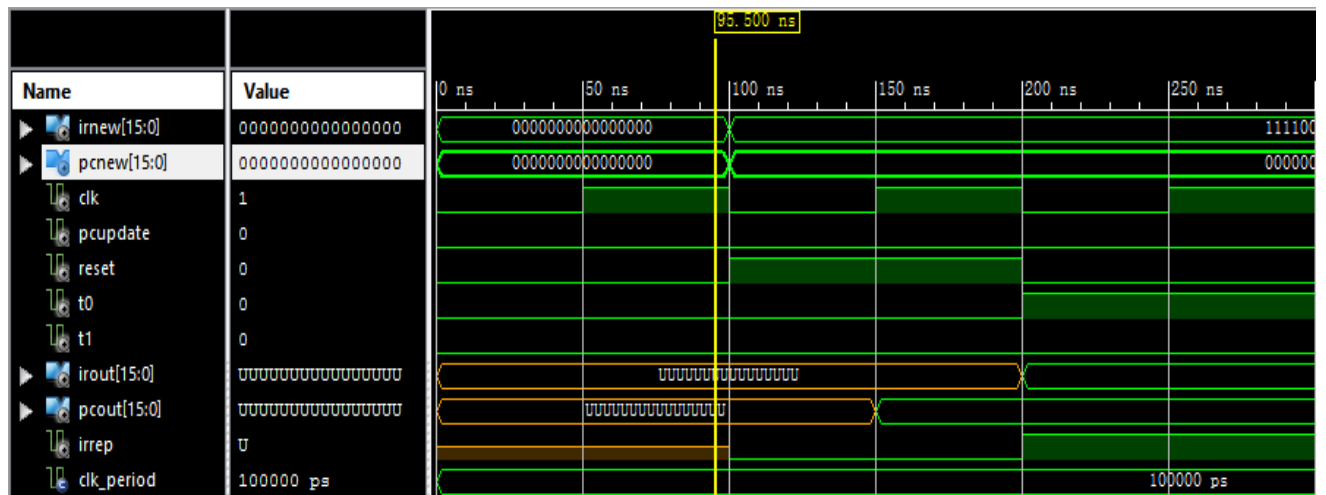

c) 运算模块

核心代码:

```

entity ALU is
port(
    -- 实现准备和运算功能
    enable_t : in std_logic ; -- 准备和运算功能使能信号
    ir : in std_logic_vector(15 downto 0);

    -- 向访存控制模块输出
    sig_reg7aluout : out std_logic_vector ( 15 downto 0 ); -- 暂存器输出端口
    sig_reg7addrout : out std_logic_vector ( 15 downto 0 ); -- 8 位地址输出端口
    --reg7_out : out std_logic_vector ( 7 downto 0 );

    -- 实现回写功能
    enable_wb : in std_logic ; -- 回写功能使能
    reg_wb : in std_logic_vector (7 downto 0 ); -- 回写接收端口

    -- 进位标志
    cy : out std_logic
);

end ALU;

```

architecture Behavioral of ALU is

```

type registers_8 is array (7 downto 0) of std_logic_vector(7 downto 0);
signal reg : registers_8; -- 数组型 8 个 8 位寄存器
signal addr : std_logic_vector ( 7 downto 0 ); -- 暂存器
begin
    get_ready : process (enable_t,addr)
    variable a,b : std_logic_vector ( 7 downto 0 );
    variable tempa , tempb ,tempsum: std_logic_vector (8 downto 0 ); -- 进位标志计算

    begin
        a := reg(conv_integer(ir(10 downto 8)));
        b := reg(conv_integer(ir(2 downto 0)));
        addr <= ir( 7 downto 0 );
        tempa := '0'&a;
        tempb := '0'&b;
        if enable_t = '1' then
            case ir(15 downto 11) is
                when "00000"=> tempsum := tempa + tempb ; --ADD
                when "00001"=> tempsum := tempa - tempb ; --SUB
            end case;
        end if;
    end get_ready;
end Behavioral;

```

```

        when "00010"=>    tempsum := tempb;                --
MOV
        when "10010"=>    tempsum := '0'&addr;            --MVI
        when "11011"=>    tempsum := '0'&addr;            --LDA
        when "11000"=>    tempsum := tempa;                --STA
        when "10001"=>    tempsum := '0'&addr;            --JMP
        when "10000"=>    tempsum := tempa;                --JZ
        --when "11111"=>    tempsum := '0'&addr;          --IN
        --when "11100"=>    tempsum :=tempa;                --


OUT
        when others=>      tempsum := "ZZZZZZZZZ";
    end case;
    sig_reg7aluout <= reg(7)&tempsum ( 7 downto 0 );
    cy <= tempsum (8) ;
    sig_reg7addrout <= reg(7)&addr;
    end if ;
end process;






write_back : process (reg_wb,enable_wb)
begin
    if enable_wb = '1' then
        reg(conv_integer(ir(10 downto 8))) <= reg_wb;
    end if;
end process;

end Behavioral;

```

## 仿真波形

 

 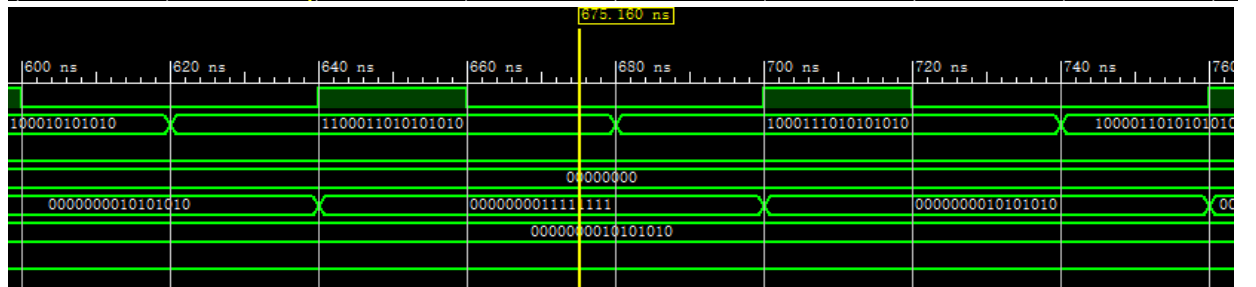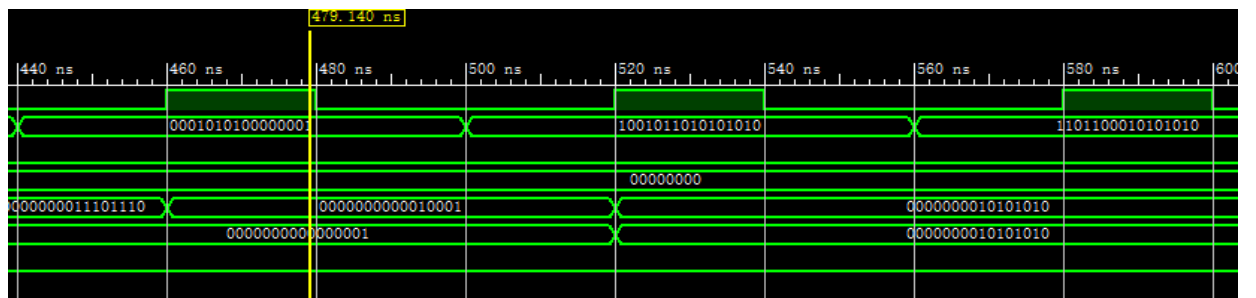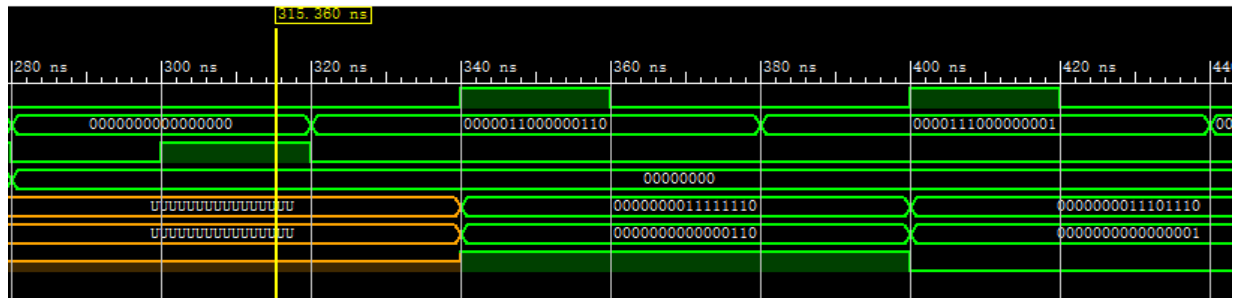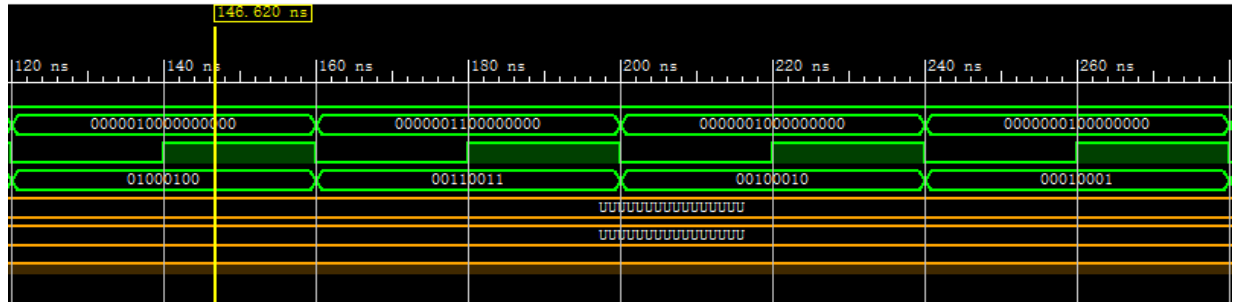

d) 存储模块




## 核心代码：

```
entity save is
  Port (
    t : in  STD_LOGIC;
    ALUOUT : in std_logic_vector(7 downto 0);    --- 取数的时候用
    data : in std_logic_vector(7 downto 0);      --- 接收区属的时候访存控
制的数据
    nMWR : out std_logic;
    IR : in  STD_LOGIC_VECTOR (15 downto 0);
    nMRD : out  STD_LOGIC;
    Rtemp : out std_logic_vector(7 downto 0));  --- 回写模块要输
end save;

architecture Behavioral of save is
begin
  process(t,data,ALUOUT,IR)
  begin
    if t = '1' then -- LDA 与 STA
      case IR(14 downto 12) is
        when "100" =>          --- STA   存数  11000
          nMWR <= '0';
          nMRD <= '1';
          Rtemp(7 downto 0) <= ALUOUT(7 downto 0);
        when "101" =>          --- LDA   取数   11011
          nMWR <= '1';
          nMRD <= '0';
          Rtemp(7 downto 0) <= data(7 downto 0);
        when others =>
          nMWR <= '1';
          nMRD <= '1';
          Rtemp(7 downto 0) <= ALUOUT(7 downto 0);
      end case;
    else
      nMWR <= '1';
      nMRD <= '1';
    end if;

    end process;
  end Behavioral;
```

## 仿真波形：

 

## e) 回写模块

### 核心代码：

```

entity write_back is
Port (
    PCin:in std_logic_vector(15 downto 0);           --接收取指模块传出的
    PC, 用于 0 跳转和直接跳转
    t : in  STD_LOGIC;                                -- 回写使能
    Rtemp : in  STD_LOGIC_VECTOR (7 downto 0);        -- 接收来自存储管理
    模块的寄存器
    IR : in  STD_LOGIC_VECTOR (15 downto 0);          -- 接收取指模块传出
    的 IR
    --z:in STD_LOGIC;                                  --接收 ALU 传出的 z
    cy:in STD_LOGIC;                                  --接收 ALU 传出的进
    位
    Rupdate : out  STD_LOGIC;                          -- 寄存器回写使能
    信号
    Rdata : out  STD_LOGIC_VECTOR (7 downto 0);        -- ALU 输出的寄存器回
    写数据
    PCupdate : out  STD_LOGIC;                        -- PC 回写使能型号
    PCnew : out  STD_LOGIC_VECTOR (15 downto 0)        --输出 PC 回写的值
);
end write_back;

architecture Behavioral of write_back is
--signal tempa:std_logic_vector(15 downto 0);
--signal tempb:std_logic_vector(15 downto 0);
begin
    -- tempa<="00000000"&(IR(7 downto 0));
    process(t, cy, IR)
    begin
        if t='1' then


```

```

case IR(15 downto 11) is
  when "10001" =>
    Rupdate <= '0'; --jmp
    PCupdate <= '1';
    PCnew <= "00000000"&(IR(7 downto 0));
  when "10000" => --jz
    Rupdate <= '0';
    if (Rtemp(7 downto 0) = "00000000") then
      --if z='1' then
        PCnew <= "00000000"&(IR(7 downto 0));
        PCupdate <= '1';
      else
        PCupdate <= '0';
      end if;
    when "11000" => null; --STA
  when others =>
    Rupdate <= '1';
    PCupdate <= '0';
    Rdata(7 downto 0) <= Rtemp(7 downto 0);
end case;
else PCupdate <= '0'; Rupdate <= '0';
end if;
end process;
end Behavioral;

```

仿真波形：

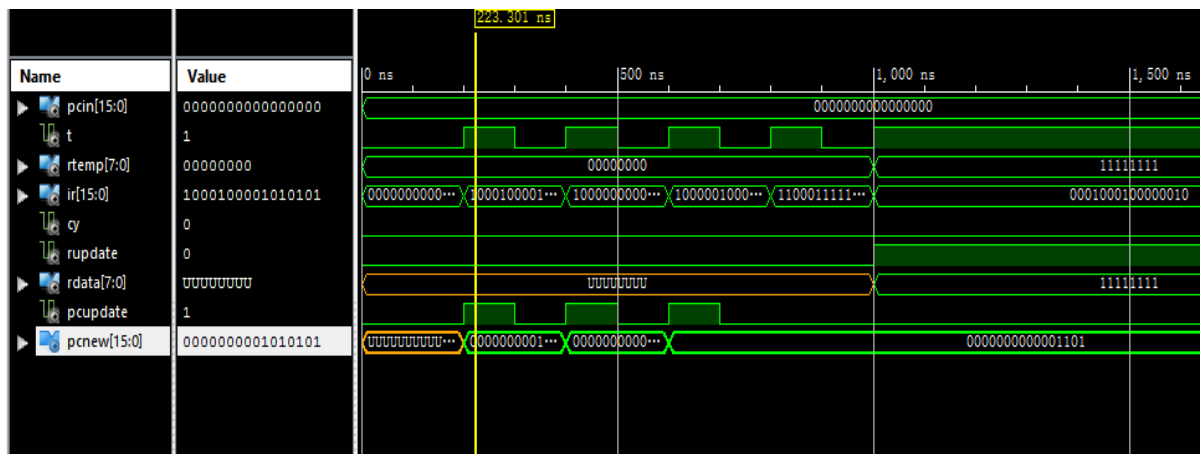

f) 访存控制模块

核心代码：

entity control is

```

port(
    IRreq :in STD_LOGIC;                --ir 使能
    IR:out  STD_LOGIC_VECTOR (15 downto 0);  --对取指模块输出 ir
    PCout: in  STD_LOGIC_VECTOR (15 downto 0);  --接收取指指令

    ALUOUT : in  STD_LOGIC_VECTOR (7 downto 0);  --运算模块
    Addr : in  STD_LOGIC_VECTOR (15 downto 0);  --运算模块

    ABUS : out  STD_LOGIC_VECTOR (15 downto 0);  --对主存输出地址
    DBUS : inout  STD_LOGIC_VECTOR (15 downto 0); --数据总线

    --给主存发
    nWR : out  STD_LOGIC;                --写主存使能
    nRD : out  STD_LOGIC;                --读主存使能
    nMREQ : out  STD_LOGIC;              --主存片选信号
    nBHE : out  STD_LOGIC;              --主存高八位控制信号
    nBLE : out  STD_LOGIC;              --主存低八位控制信号
    --运算模块/取指模块给出，要不要访内存
    nMWR : in  STD_LOGIC;                --ALU 写数使能
    nMRD : in  STD_LOGIC;                --ALU 取数使能
    --来自存储模块
    data : out  STD_LOGIC_VECTOR (7 downto 0)  --对存储控制输出取到的
数据。
);
end control;
architecture Behavioral of control is

begin
    --IR <= DBUS;
    --DBUS<="00000000"&ALUOUT when nMWR='0' else "ZZZZZZZZZZZZZZZZ";
    --data <= DBUS(7 downto 0) when nMRD = '0' else "ZZZZZZZZ";
    --ABUS<=PCout when IRreq='1' else Addr;
process(IRreq,nMRD,nMWR)
begin
    DBUS<="ZZZZZZZZZZZZZZZZ";
    if IRreq ='1' then    --取指模块
        nBHE <= '0';
        nBLE <= '0';--高低位
        nMREQ <= '0';
        nWR <= '1';
        nRD <= '0';--读有效，低电位有效
        IR <= DBUS;
        --DBUS<="ZZZZZZZZZZZZZZZZ";
        ABUS<=PCout;
    end if;
end process;
end Behavioral;

```

elsif nMRD = '0' then --需要读内存(运算模块)---读取使能，低电平有


elseif nMWR = '0' then --写内存(运算模块)


else

end if;

end Behavioral;

仿真波形:

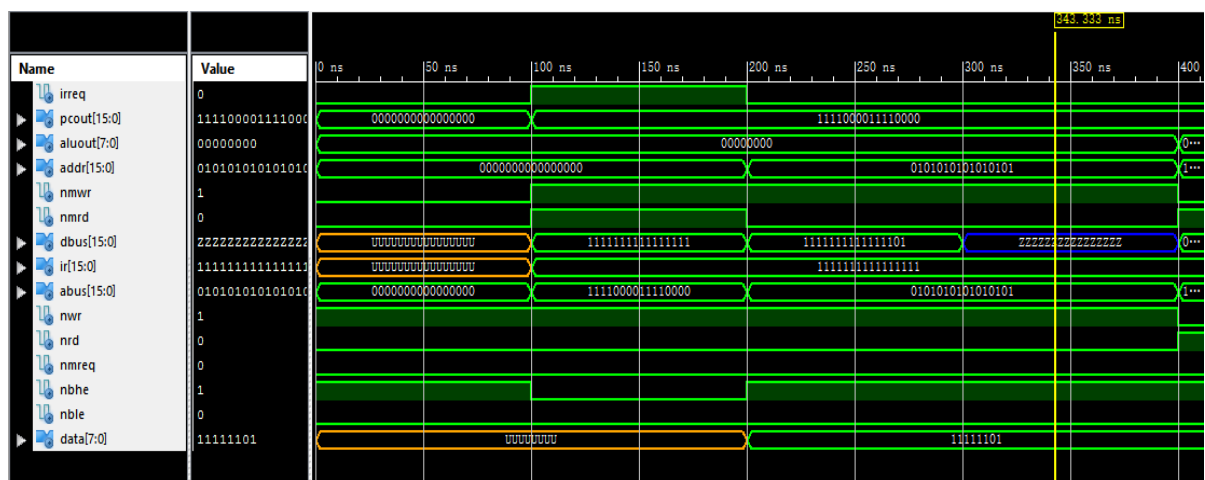

 

## g) 总体波形仿真

### 核心代码：

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity CPU is
    Port ( RST : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          ABUS : out  STD_LOGIC_VECTOR (15 downto 0);
          DBUS : inout  STD_LOGIC_VECTOR (15 downto 0);
          nMREQ : out  STD_LOGIC;
          nRD : out  STD_LOGIC;
          nWR : out  STD_LOGIC;
          nBHE : out  STD_LOGIC;
          nBLE : out  STD_LOGIC);
end CPU;

architecture Behavioral of CPU is
    component clock is
        port (
            clk : in  STD_LOGIC;
```

```

        reset : in  STD_LOGIC;
        t : out  STD_LOGIC_VECTOR (4 downto 0)
    );
end component;

component fetch is
    port (
        irnew : in  STD_LOGIC_VECTOR (15 downto 0);           --访存模
块输入的 IR
        pcnew : in  STD_LOGIC_VECTOR (15 downto 0);           --回写模
块, 更新 PC
        clk : in  STD_LOGIC;                                   --节拍
        pcupdate : in  STD_LOGIC;                             --告诉要更
新 PC 了
        reset : in  STD_LOGIC;                                 --复位
        t0 : in  STD_LOGIC;
        t1 : in  STD_LOGIC;
        irout : out  STD_LOGIC_VECTOR (15 downto 0);          --输出的 IR
        pcout : out  STD_LOGIC_VECTOR (15 downto 0);
        irrep : out  STD_LOGIC
    );
end component;

component ALU is
    port (
        -- 实现准备和运算功能
        enable_t : in std_logic; -- 准备和运算功能使能信号
        ir : in std_logic_vector(15 downto 0);    --16 位的 IR 信号

        -- 向访存控制模块输出
        sig_reg7aluout : out std_logic_vector ( 15 downto 0 ); -- 暂存器输
出端口
        sig_reg7addrout : out std_logic_vector ( 15 downto 0 ); -- 8 位地址
输出端口
        --reg7_out : out std_logic_vector ( 7 downto 0 );

        -- 实现回写功能
        enable_wb : in std_logic ; -- 回写功能使能
        reg_wb : in std_logic_vector (7 downto 0 ); -- 回写接收端口

        -- 进位标志
        cy : out std_logic
    );
end component;

```

```

component control is
    port (
        IRreq :in STD_LOGIC;                --ir 使能
        IR:out  STD_LOGIC_VECTOR (15 downto 0);    --对取指模块
输出 ir
        PCout: in  STD_LOGIC_VECTOR (15 downto 0);    --接收取指指
令
        ALUOUT : in  STD_LOGIC_VECTOR (7 downto 0);    --运算模块
        Addr : in  STD_LOGIC_VECTOR (15 downto 0);    --运算模块

        ABUS : out  STD_LOGIC_VECTOR (15 downto 0);    --对主存输出
地址
        DBUS : inout  STD_LOGIC_VECTOR (15 downto 0); --数据总线

        --给主存发
        nWR : out  STD_LOGIC;                --写主存使
能
        nRD : out  STD_LOGIC;                --读主存使
能
        nMREQ : out  STD_LOGIC;            --主存片选
信号
        nBHE : out  STD_LOGIC;            --主存高八
位控制信号
        nBLE : out  STD_LOGIC;            --主存低八
位控制信号
        --运算模块/取指模块给出，要不要访内存
        nMWR : in  STD_LOGIC;                --ALU 写
数使能
        nMRD : in  STD_LOGIC;                --ALU 取数
使能
        --来自存储模块
        data : out  STD_LOGIC_VECTOR (7 downto 0)    --对存储控制
输出取到的数据。
    );
end component;

```

```

component save is
    port (
        t : in  STD_LOGIC;
        ALUOUT : in std_logic_vector(7 downto 0);    --- ALU 输出的值
        data : in std_logic_vector(7 downto 0);    --- 接收区属的时
候访存控制的数据

```



```

        nMWR : out std_logic;
        IR : in  STD_LOGIC_VECTOR (15 downto 0);
        nMRD : out  STD_LOGIC;
        Rtemp : out std_logic_vector(7 downto 0)
    );
end component;

component write_back is
    port (
        PCin:in std_logic_vector(15 downto 0);           --接收取指模
        块传出的 PC，用于 0 跳转和直接跳转
        t : in  STD_LOGIC;                                -- 回写
        使能
        Rtemp : in  STD_LOGIC_VECTOR (7 downto 0);        -- 接收来
        自存储管理模块的寄存器
        IR : in  STD_LOGIC_VECTOR (15 downto 0);          -- 接收取
        指模块传出的 IR
        --z:in STD_LOGIC;                                  --接收
        ALU 传出的 z
        cy:in STD_LOGIC;                                   --接收
        ALU 传出的进位
        Rupdate : out  STD_LOGIC;                          -- 寄存
        器回写使能信号
        Rdata : out  STD_LOGIC_VECTOR (7 downto 0);        -- ALU 输
        出的寄存器回写数据
        PCupdate : out  STD_LOGIC;                          -- PC 回
        写使能信号
        PCnew : out  STD_LOGIC_VECTOR (15 downto 0)        --输出 PC
        回写的值
    );
end component;

signal t : STD_LOGIC_VECTOR(4 downto 0);                --正常节拍
signal IR_C_F : STD_LOGIC_VECTOR(15 downto 0);         -- 取指模块取出的 ir
signal PCout_F_CW : STD_LOGIC_VECTOR(15 downto 0);     -- PC 送往访存控制取
指，送回写模块
signal PCnew_W_F : STD_LOGIC_VECTOR(15 downto 0);      -- 跳转的时候要更
新的 PC
signal PCupdate_W_F : STD_LOGIC;                        -- 跳转更新 PC 使能
信号
signal irout_F_ASF : STD_LOGIC_VECTOR(15 downto 0);    --取指模块取到的 Ir,会
送往 ALU 存储 和回写
signal irreq_F_C : STD_LOGIC;                          -- 取指送往访存控制，告诉
要取指令了

```

```

signal ALUOUT_A_CS : STD_LOGIC_VECTOR(15 downto 0);    ---ALU 送往其他模
块的 aluout
signal Addr_A_C : STD_LOGIC_VECTOR(15 downto 0);        --- ALU 送往访存的
addr
signal Rupdate_W_A : STD_LOGIC;                          ---回写模块送往
ALU 的更改寄存器使能信号
signal Rdata_W_A : STD_LOGIC_VECTOR(7 downto 0);        ----回写模块输出
的要更新的寄存器的值
signal data_C_S : STD_LOGIC_VECTOR(7 downto 0);          -- 取数的时候使
用
signal nMWR_S_C : STD_LOGIC;                             --写数使能
signal nMRD_S_C : STD_LOGIC;                             --读数使能
signal Rtemp_S_W : STD_LOGIC_VECTOR(7 downto 0);        -- 存储模块向
回写模块
signal cy_A_W : STD_LOGIC;                               --进位


begin





    u1: clock port map(CLK, RST, t);
    u2: fetch port map(IR_C_F, PCnew_W_F, CLK , PCupdate_W_F, RST, t(0), t(1),
irout_F_ASW, PCout_F_CW, irreq_F_C);
    u3: ALU port map(t(2), irout_F_ASW, ALUOUT_A_CS, Addr_A_C,
Rupdate_W_A, Rdata_W_A, cy_A_W);
    u4: control port map(irreq_F_C, IR_C_F, PCout_F_CW, ALUOUT_A_CS(7
downto 0), Addr_A_C, ABUS, DBUS, nWR, nRD, nMREQ, nBHE, nBLE, nMWR_S_C,
nMRD_S_C , data_C_S);
    u5: save port map(t(3), ALUOUT_A_CS(7 downto 0), data_C_S, nMWR_S_C,
irout_F_ASW, nMRD_S_C, Rtemp_S_W);
    u6: write_back port map(PCout_F_CW, t(4), Rtemp_S_W, irout_F_ASW,
cy_A_W, Rupdate_W_A, Rdata_W_A, PCupdate_W_F, PCnew_W_F);





end Behavioral;





```


仿真波形：




 


  
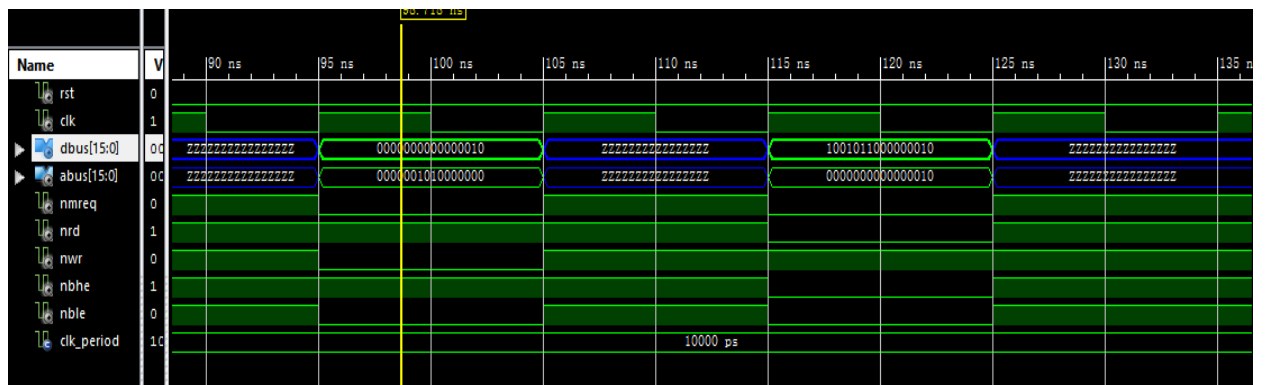
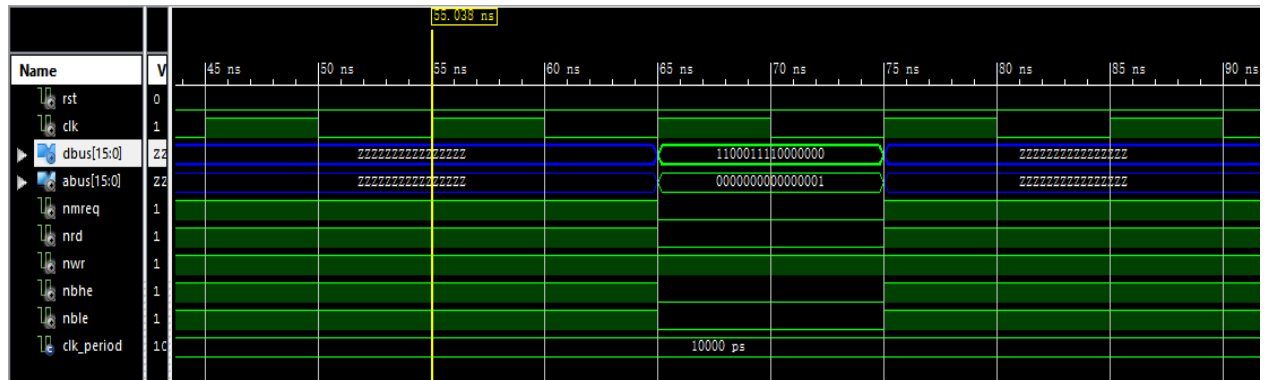


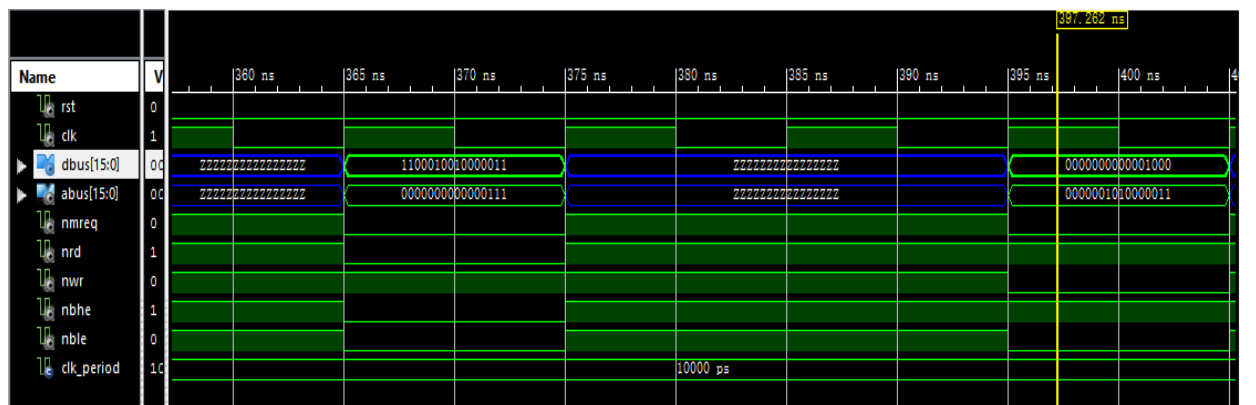   

 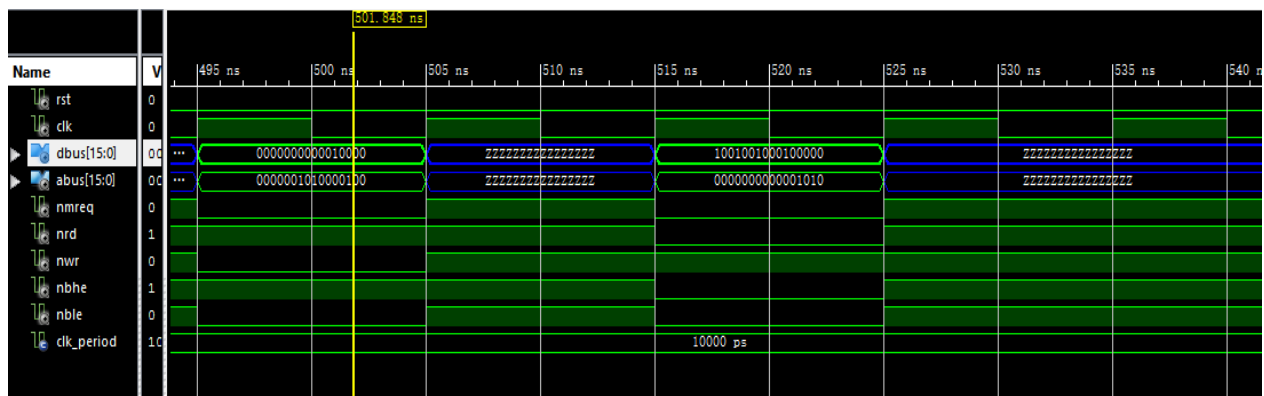
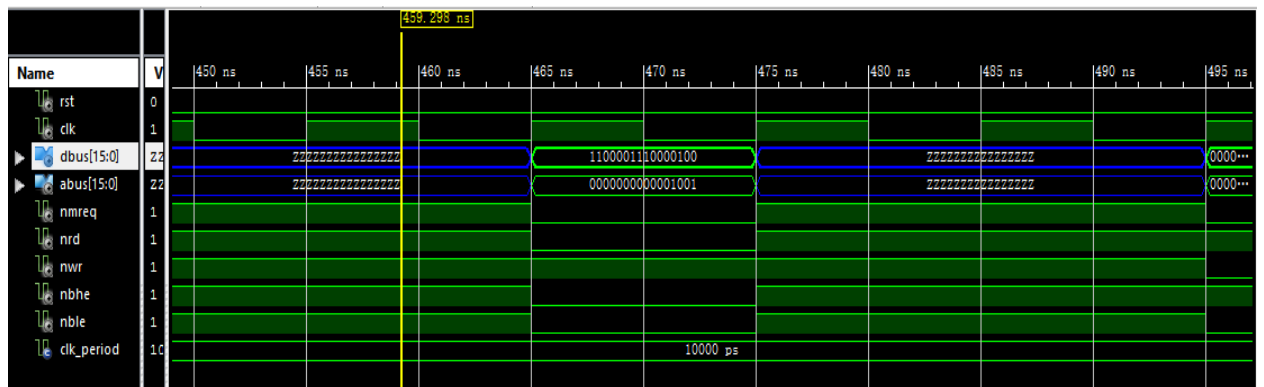
 





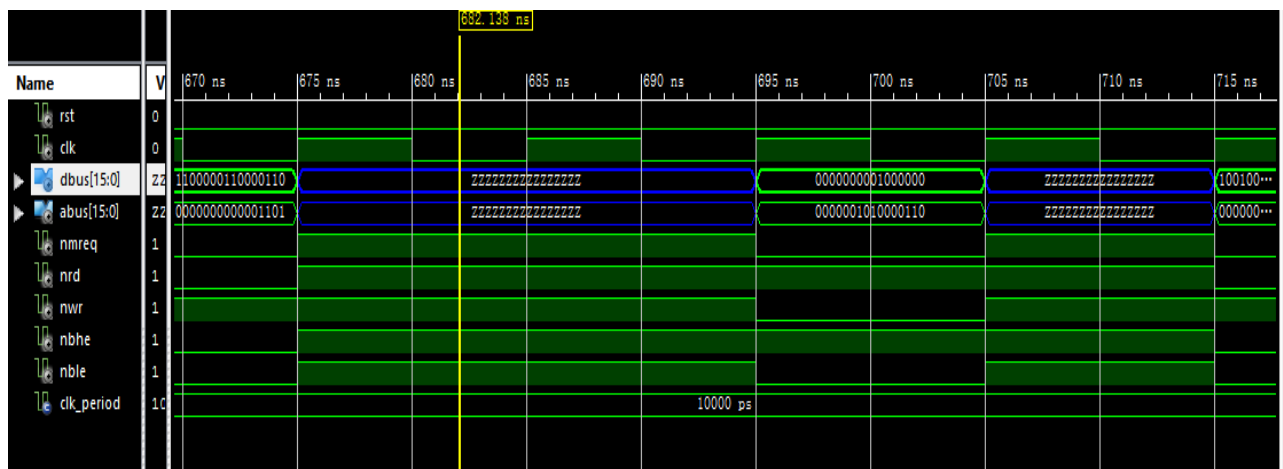


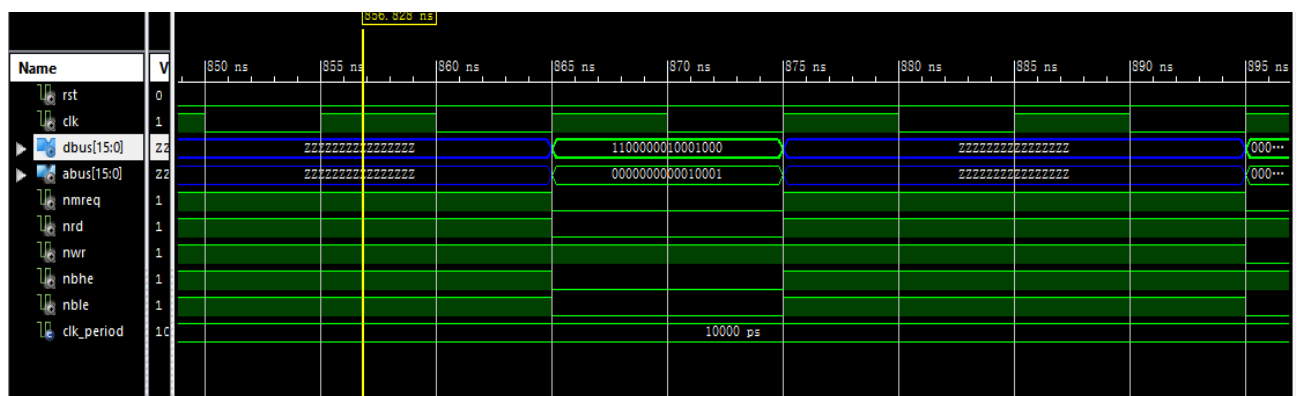
 
 
 


 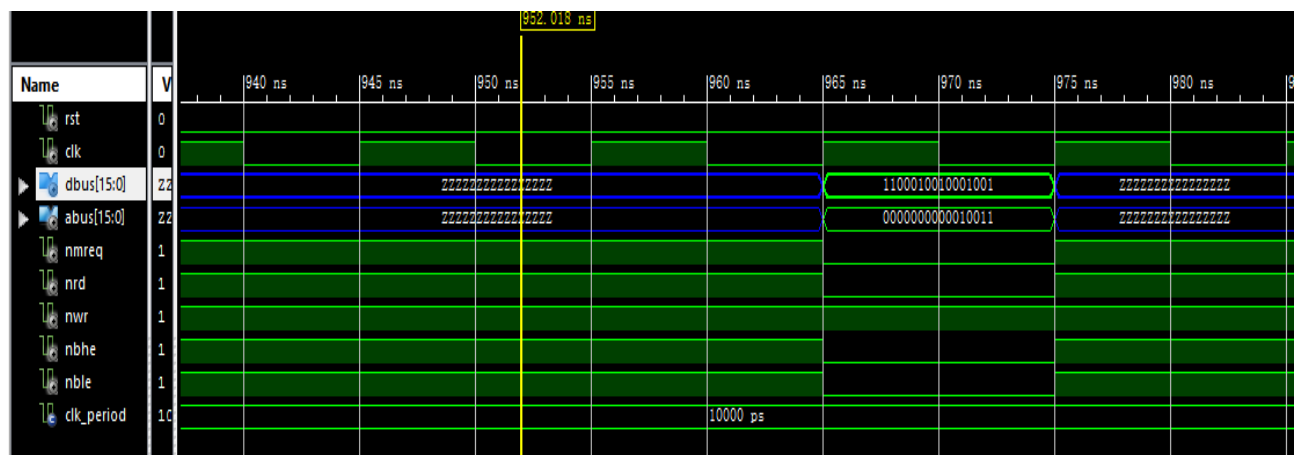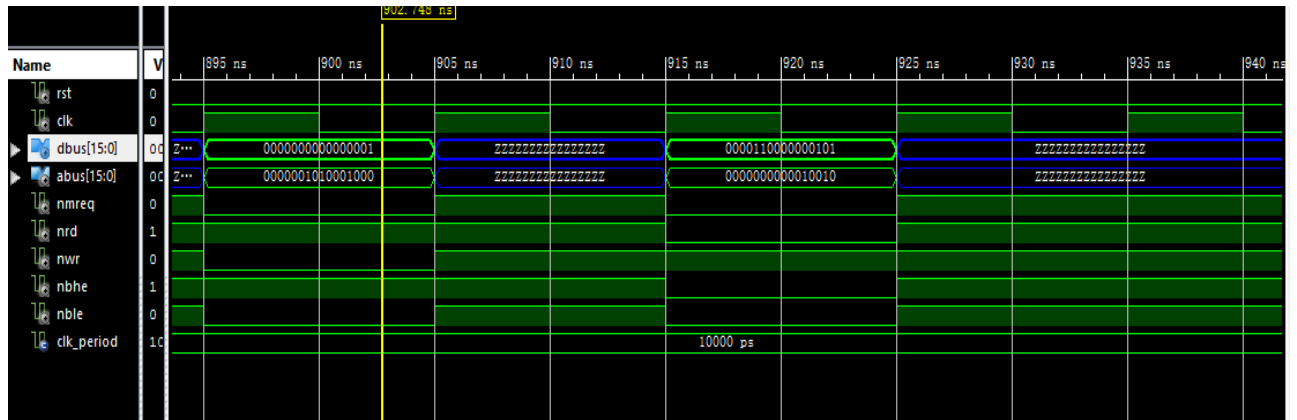




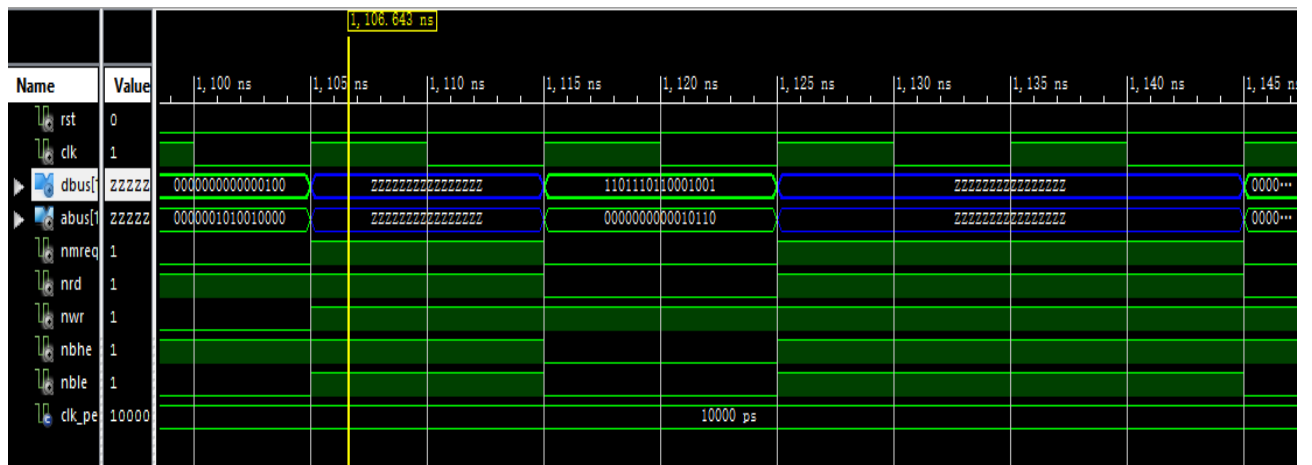  

 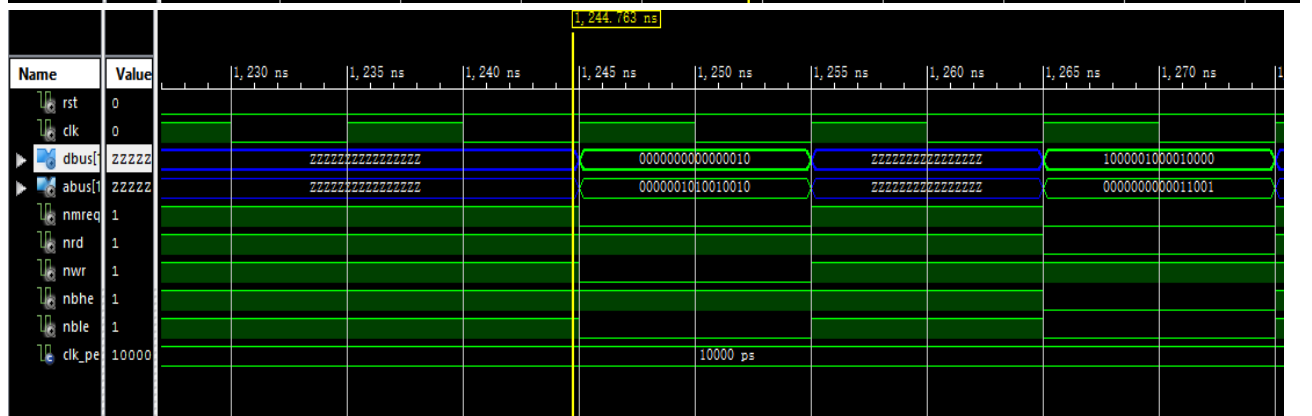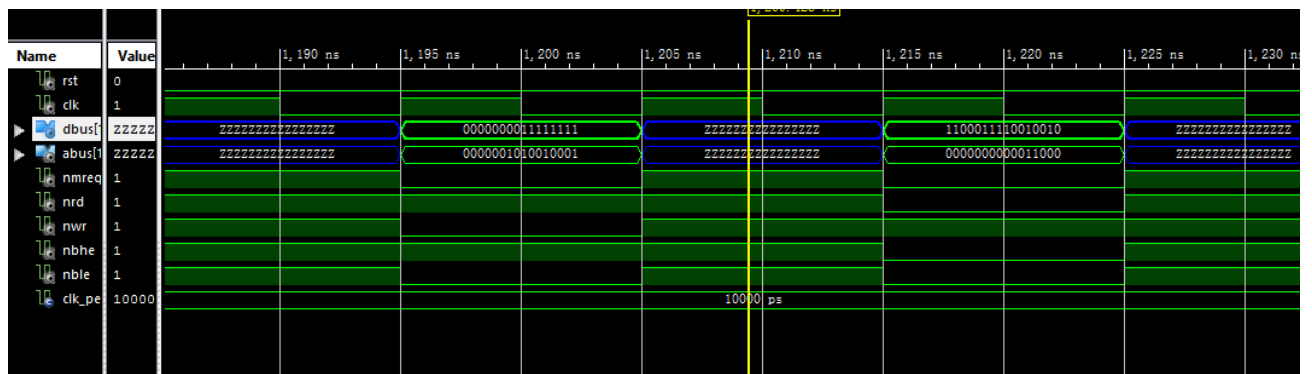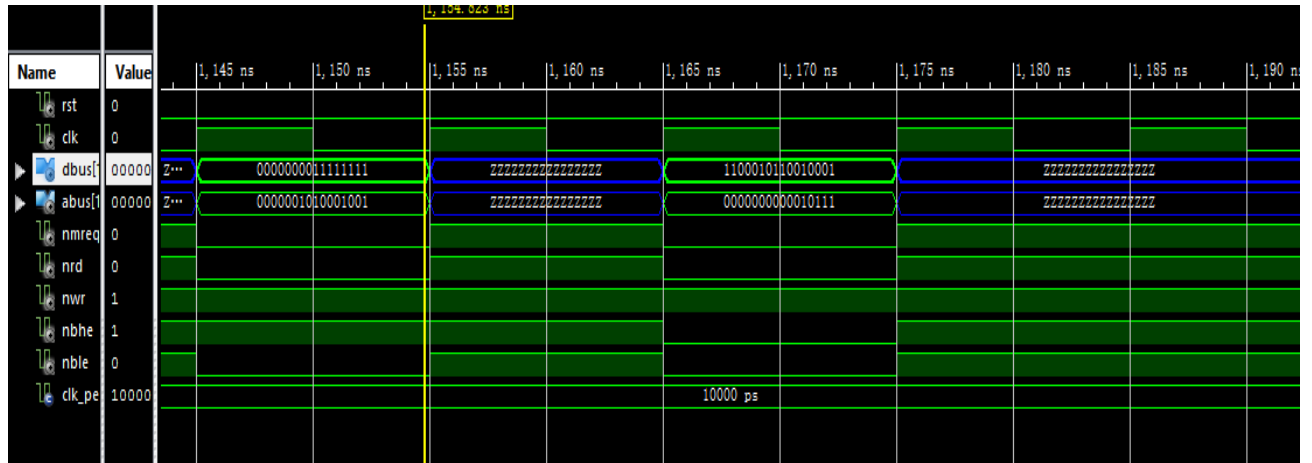

 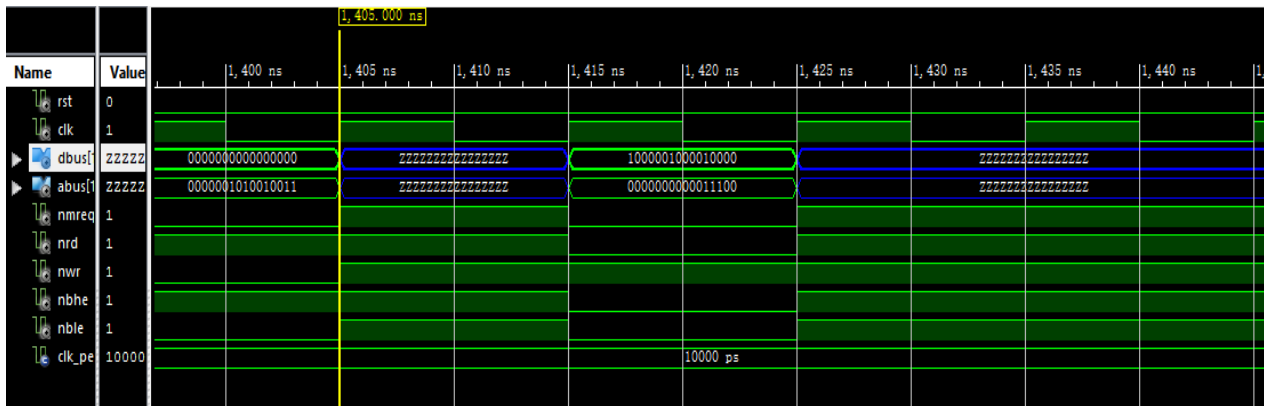  

 

## 实验感想

1. **设计过程：**在刚开始的设计中，出现了对整体的把握不是特别严谨的问题，尤其是在访存这块出现了比较严重的问题，没有比较好的理清几个访存操作，致使在写 VHDL 的过程中一直不能比较好的解决问题。
2. **调试过程：**数据总线采用的是 inout 类型，但是在整个过程中对 inout 的理解不是很好，在老师的辅导和同学的帮助中才慢慢的开始理解他，最后解决了问题。
3. **下载过程：**本以为总的仿真波形没有问题之后可以很快的下载到开发板上，结果就在生成 bit 文件的时候遇到了闭门羹——直接无法生成 bit 文件，遇到了 93 错误，还好在老师的提醒下修改了取指阶段的代码，让每一个 process 负责一个信号，即把 pc 和 ir 分来，放在两个 Process 中。接下来的过程还是遇到了很多奇怪的问题，出现了往主存中写数写不出的错误，最后在老师的帮助下对一些信号接上了等，逐一去查找错误，最后发现问题出现在回写阶段，才比较好的解决了问题。

**总的来说：**虽然实验台比较老旧，甚至有的设备直接无法工作。但这次实验室特别有用的，自己开始按照自己的一些思路去设计 CPU，比较好的复习了计算机组成原理中的一些东西，也对 CPU 有了更深层次的认识。

## 附测试代码：

### Clock\_tb:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY clock_tb IS
END clock_tb;

ARCHITECTURE behavior OF clock_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT clock
    PORT(
        clk : IN    std_logic;
        reset : IN   std_logic;
        t : OUT  std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal clk : std_logic := '0';
    signal reset : std_logic := '0';

    --Outputs
    signal t : std_logic_vector(3 downto 0);

    -- Clock period definitions
    constant clk_period : time := 100 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: clock PORT MAP (
        clk => clk,
        reset => reset,
        t => t
    );
```

```

    );

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    reset <= '1';
    wait for 100 ns;
    reset <= '0';
    wait for clk_period*10;
    wait for 100ns;
    reset <= '1';
    -- insert stimulus here

    wait;
end process;

END;

```

## Fetch\_tb:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY fetch_tb IS
END fetch_tb;

ARCHITECTURE behavior OF fetch_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

```

```

COMPONENT fetch
PORT(
    irnew : IN    std_logic_vector(15 downto 0);
    pcnew : IN    std_logic_vector(15 downto 0);
    clk : IN    std_logic;
    pcupdate : IN    std_logic;
    reset : IN    std_logic;
    t0 : IN    std_logic;
    t1 : IN    std_logic;
    irout : OUT    std_logic_vector(15 downto 0);
    pcout : OUT    std_logic_vector(15 downto 0);
    irrep : OUT    std_logic
);
END COMPONENT;

```

--Inputs

```

signal irnew : std_logic_vector(15 downto 0) := (others => '0');
signal pcnew : std_logic_vector(15 downto 0) := (others => '0');
signal clk : std_logic := '0';
signal pcupdate : std_logic := '0';
signal reset : std_logic := '0';
signal t0 : std_logic := '0';
signal t1 : std_logic := '0';

```

--Outputs

```

signal irout : std_logic_vector(15 downto 0);
signal pcout : std_logic_vector(15 downto 0);
signal irrep : std_logic;

```

-- Clock period definitions

```

constant clk_period : time := 100 ns;

```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```

uut: fetch PORT MAP (
    irnew => irnew,
    pcnew => pcnew,
    clk => clk,
    pcupdate => pcupdate,
    reset => reset,
    t0 => t0,
    t1 => t1,

```

```

        irout => irout,
        pcout => pcout,
        irrep => irrep
    );

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100ns;
    reset <= '1';
    t0 <= '0';
    t1 <= '0';
    pcupdate <= '0';
    irnew <= "1111000011110000";
    pcnew <= "0000000011111111";

    wait for 100ns;
    reset <= '0';
    t0 <= '1';
    wait for 100ns;
    t0 <= '0';
    --pcupdate <= '1';
    wait for 150ns;
    pcupdate <= '0';
    t1 <= '1';
    wait for 100ns;
    --下面一行是刚才修改的
    t0 <= '1';
    pcupdate <= '1';
    t1 <= '0';
    wait for 100ns;
    reset <= '1';

```



```
wait for clk_period*10;
```

```
-- insert stimulus here
```

```
wait;  
end process;
```

```
END;
```

## ALU\_tb:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--USE ieee.numeric_std.ALL;
```

```
ENTITY ALU_tb IS
```

```
END ALU_tb;
```

```
ARCHITECTURE behavior OF ALU_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT ALU
```

```
PORT(
```

```
    enable_t : IN    std_logic;
```

```
    ir : IN std_logic_vector(15 downto 0);
```

```
    sig_reg7aluout : OUT  std_logic_vector(15 downto 0);
```

```
    sig_reg7addrout : OUT  std_logic_vector(15 downto 0);
```

```
    enable_wb : IN    std_logic;
```

```
    reg_wb : IN    std_logic_vector(7 downto 0);
```

```
    cy : OUT  std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal enable_t : std_logic := '0';
```

```
    signal ir : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal enable_wb : std_logic := '0';
```

```
signal reg_wb : std_logic_vector(7 downto 0) := (others => '0');
```

```

--Outputs
signal sig_reg7aluout : std_logic_vector(15 downto 0);
signal sig_reg7addrout : std_logic_vector(15 downto 0);
signal cy : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

```

```

BEGIN

```

```

-- Instantiate the Unit Under Test (UUT)
uut: ALU PORT MAP (
    enable_t => enable_t,
    ir => ir,
    sig_reg7aluout => sig_reg7aluout,
    sig_reg7addrout => sig_reg7addrout,
    enable_wb => enable_wb,
    reg_wb => reg_wb,
    cy => cy
);

```

```

-- Stimulus process
stim_proc: process
begin
    -- 测试回写模
    ir <= "0000011100000000";
    reg_wb <= "00000000";
    enable_wb <= '0';
    wait for 20 ns;
    enable_wb <= '1';
    wait for 20 ns;

```

```

    ir <= "0000011000000000";
    reg_wb <= "11111111";
    enable_wb <= '0';
    wait for 20 ns;
    enable_wb <= '1';
    wait for 20 ns;

```

```

    ir <= "0000010100000000";
    reg_wb <= "11111111";
    enable_wb <= '0';

```

```
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;
```

```
ir <= "0000010000000000";  
reg_wb <= "01000100";  
enable_wb <= '0';  
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;
```

```
ir <= "0000001100000000";  
reg_wb <= "00110011";  
enable_wb <= '0';  
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;
```

```
ir <= "0000001000000000";  
reg_wb <= "00100010";  
enable_wb <= '0';  
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;
```

```
ir <= "0000000100000000";  
reg_wb <= "00010001";  
enable_wb <= '0';  
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;
```

```
ir <= "0000000000000000";  
reg_wb <= "00000000";  
enable_wb <= '0';  
wait for 20 ns;  
enable_wb <= '1';  
wait for 20 ns;  
enable_wb <= '0';
```

-- 测试操作码，同时测试进位标志

--ADD

ir <= "0000011000000110";

enable\_t <= '0';

wait for 20 ns ;

enable\_t <= '1';

wait for 20 ns ;

enable\_t <= '0' ;

wait for 20 ns;

--SUB

ir <= "0000111000000001";

enable\_t <= '0';

wait for 20 ns ;

enable\_t <= '1';

wait for 20 ns ;

enable\_t <= '0' ;

wait for 20 ns;

--MOV

ir <= "0001010100000001";

enable\_t <= '0';

wait for 20 ns ;

enable\_t <= '1';

wait for 20 ns ;

enable\_t <= '0' ;

wait for 20 ns;

--MVI

ir <= "1001011010101010";

enable\_t <= '0';

wait for 20 ns ;

enable\_t <= '1';

wait for 20 ns ;

enable\_t <= '0' ;

wait for 20 ns;

--LDA

ir <= "1101100010101010";

enable\_t <= '0';

wait for 20 ns ;

enable\_t <= '1';

wait for 20 ns ;

```

        enable_t <= '0' ;
        wait for 20 ns;

--STA
        ir <= "1100011010101010";
        enable_t <= '0';
        wait for 20 ns ;
        enable_t <= '1';
        wait for 20 ns ;
        enable_t <= '0' ;
        wait for 20 ns;

--JMP
        ir <= "1000111010101010";
        enable_t <= '0';
        wait for 20 ns ;
        enable_t <= '1';
        wait for 20 ns ;
        enable_t <= '0' ;
        wait for 20 ns;

--JZ
        ir <= "1000011010101010";
        enable_t <= '0';
        wait for 20 ns ;
        enable_t <= '1';
        wait for 20 ns ;
        enable_t <= '0' ;
        wait for 20 ns;

        wait;
    end process;

```

```
END;
```

## Control\_tb:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY control_tb IS

```

```
END control_tb;
```

```
ARCHITECTURE behavior OF control_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT control
```

```
PORT(
```

```
    IRreq : IN    std_logic;  
    IR : OUT  std_logic_vector(15 downto 0);  
    PCout : IN  std_logic_vector(15 downto 0);  
    ALUOUT : IN  std_logic_vector(7 downto 0);  
    Addr : IN  std_logic_vector(15 downto 0);  
    ABUS : OUT  std_logic_vector(15 downto 0);  
    DBUS : INOUT std_logic_vector(15 downto 0);  
    nWR : OUT  std_logic;  
    nRD : OUT  std_logic;  
    nMREQ : OUT std_logic;  
    nBHE : OUT  std_logic;  
    nBLE : OUT  std_logic;  
    nMWR : IN  std_logic;  
    nMRD : IN  std_logic;  
    data : OUT  std_logic_vector(7 downto 0)  
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal IRreq : std_logic := '0';  
signal PCout : std_logic_vector(15 downto 0) := (others => '0');  
signal ALUOUT : std_logic_vector(7 downto 0) := (others => '0');  
signal Addr : std_logic_vector(15 downto 0) := (others => '0');  
signal nMWR : std_logic := '0';  
signal nMRD : std_logic := '0';
```

```
--BiDirs
```

```
signal DBUS : std_logic_vector(15 downto 0);
```

```
--Outputs
```

```
signal IR : std_logic_vector(15 downto 0);  
signal ABUS : std_logic_vector(15 downto 0);  
signal nWR : std_logic;  
signal nRD : std_logic;  
signal nMREQ : std_logic;
```

```

signal nBHE : std_logic;
signal nBLE : std_logic;
signal data : std_logic_vector(7 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

```

```

BEGIN

```

```

    -- Instantiate the Unit Under Test (UUT)

```

```

    uut: control PORT MAP (
        IRreq => IRreq,
        IR => IR,
        PCout => PCout,
        ALUOUT => ALUOUT,
        Addr => Addr,
        ABUS => ABUS,
        DBUS => DBUS,
        nWR => nWR,
        nRD => nRD,
        nMREQ => nMREQ,
        nBHE => nBHE,
        nBLE => nBLE,
        nMWR => nMWR,
        nMRD => nMRD,
        data => data
    );

```

```

    -- Stimulus process

```

```

    stim_proc: process

```

```

    begin

```

```

        -- hold reset state for 100 ns

```

```

        --- ??

```

```

        wait for 100 ns;

```

```

        nMRD <= '1';

```

```

        nMWR <= '1';

```

```

        DBUS <= "1111111111111111";

```

```

        IRreq <= '1';

```

```

        PCout <= "1111000011110000";

```

```

wait for 100 ns;
IRreq <= '0';
nMRD <= '0';
DBUS <= "111111111111101";
Addr <= "0101010101010101";

wait for 100 ns;
DBUS <= "ZZZZZZZZZZZZZZZZ"; --gaozu

wait for 100 ns;
nMRD <= '1';
nMWR <= '0';
ALUOUT <= "00001111";
Addr <= "1010101010101010";

```

```

wait;
end process;

```

```
END;
```

## Save\_tb:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY save_tb IS
END save_tb;

ARCHITECTURE behavior OF save_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT save
    PORT(
        t : IN    std_logic;
        ALUOUT : IN    std_logic_vector(7 downto 0);
        data : IN    std_logic_vector(7 downto 0);
        nMWR : OUT    std_logic;
        IR : IN    std_logic_vector(15 downto 0);
        nMRD : OUT    std_logic;

```



```
        Rtemp : OUT    std_logic_vector(7 downto 0)
    );
END COMPONENT;
```

--Inputs

```
signal t : std_logic := '0';
signal ALUOUT : std_logic_vector(7 downto 0) := (others => '0');
signal data : std_logic_vector(7 downto 0) := (others => '0');
signal IR : std_logic_vector(15 downto 0) := (others => '0');
```

--Outputs

```
signal nMWR : std_logic;
signal nMRD : std_logic;
signal Rtemp : std_logic_vector(7 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: save PORT MAP (
    t => t,
    ALUOUT => ALUOUT,
    data => data,
    nMWR => nMWR,
    IR => IR,
    nMRD => nMRD,
    Rtemp => Rtemp
);
```

-- Stimulus process

```
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    t <= '0';
    wait for 100 ns;
    t <= '1';
    IR <= "1101100000000000";    --取数
    data <= "01010011";
```

```

        wait for 100 ns;
        IR <= "1100000000000000";    --存数
        ALUOUT <= "11110000";
        -- insert stimulus here

        wait;
    end process;

END;

```

## Write\_back\_tb:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY write_back_tb IS
END write_back_tb;

ARCHITECTURE behavior OF write_back_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT write_back
    PORT(
        PCin : IN    std_logic_vector(15 downto 0);
        t : IN    std_logic;
        Rtemp : IN    std_logic_vector(7 downto 0);
        IR : IN    std_logic_vector(15 downto 0);
        z : IN    std_logic;
        cy : IN    std_logic;
        Rupdate : OUT    std_logic;
        Rdata : OUT    std_logic_vector(7 downto 0);
        PCupdate : OUT    std_logic;
        PCnew : OUT    std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal PCin : std_logic_vector(15 downto 0) := (others => '0');
    signal t : std_logic := '0';

```

```
signal Rtemp : std_logic_vector(7 downto 0) := (others => '0');
signal IR : std_logic_vector(15 downto 0) := (others => '0');
signal z : std_logic := '0';
signal cy : std_logic := '0';
```

--Outputs

```
signal Rupdate : std_logic;
signal Rdata : std_logic_vector(7 downto 0);
signal PCupdate : std_logic;
signal PCnew : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: write_back PORT MAP (
    PCin => PCin,
    t => t,
    Rtemp => Rtemp,
    IR => IR,
    z => z,
    cy => cy,
    Rupdate => Rupdate,
    Rdata => Rdata,
    PCupdate => PCupdate,
    PCnew => PCnew
);
```

-- Stimulus process

```
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    t <= '0';

    wait for 100 ns;
    t <= '1'; ---JMP
    IR <= "1000100001010101";
```

```

wait for 100 ns;
t <= '0';

wait for 100 ns;
t <= '1';
IR <= "1000000000001111";
z <= '1';

wait for 100 ns;
t <= '0';

wait for 100 ns;
t <= '1';
IR <= "1000001000001101";
z <= '0';

wait for 100 ns;
t <= '0';

wait for 100 ns;
t <= '1';
IR <= "1100011111110000";    -- STA

wait for 100 ns;
t <= '0';

wait for 100 ns;
t <= '1';
IR <= "0001000100000010";
Rtemp <= "11111111";
-- insert stimulus here

wait;
end process;

```

```
END;
```

## CPU\_tb:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

```

```
ENTITY CPU_tb IS
```

```
END CPU_tb;
```

```
ARCHITECTURE behavior OF CPU_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT CPU
```

```
PORT(
```

```
    RST : IN    std_logic;
```

```
    CLK : IN    std_logic;
```

```
    ABUS : OUT   std_logic_vector(15 downto 0);
```

```
    DBUS : INOUT std_logic_vector(15 downto 0);
```

```
    nMREQ : OUT  std_logic;
```

```
    nRD : OUT   std_logic;
```

```
    nWR : OUT   std_logic;
```

```
    nBHE : OUT  std_logic;
```

```
    nBLE : OUT  std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal RST : std_logic := '0';
```

```
signal CLK : std_logic := '0';
```

```
--BiDirs
```

```
signal DBUS : std_logic_vector(15 downto 0);
```

```
--Outputs
```

```
signal ABUS : std_logic_vector(15 downto 0);
```

```
signal nMREQ : std_logic;
```

```
signal nRD : std_logic;
```

```
signal nWR : std_logic;
```

```
signal nBHE : std_logic;
```

```
signal nBLE : std_logic;
```

```
-- Clock period definitions
```

```
constant CLK_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```

    uut: CPU PORT MAP (
        RST => RST,
        CLK => CLK,
        ABUS => ABUS,
        DBUS => DBUS,
        nMREQ => nMREQ,
        nRD => nRD,
        nWR => nWR,
        nBHE => nBHE,
        nBLE => nBLE
    );

-- Clock process definitions
CLK_process :process
begin
    CLK <= '0';
    wait for CLK_period/2;
    CLK <= '1';
    wait for CLK_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    --复位
    RST <= '1';
    DBUS <= "ZZZZZZZZZZZZZZZZZZ";

    wait for 10 ns;
    RST <= '0';
    wait for 5 ns;
    DBUS <= "1001011100000010";          --- MVI R7  00000000

9700
    wait for 10 ns;
    DBUS <= "ZZZZZZZZZZZZZZZZZZ";
    wait for 40 ns;

    DBUS <= "1100011110000000";          --- STA R7 80h      c780
    wait for 10 ns;
    DBUS <= "ZZZZZZZZZZZZZZZZZZ";
    wait for 40 ns;

```

9600	DBUS <= "1001011000000010"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- MVI R6 00000010
c681	DBUS <= "1100011010000001"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- STA R6 81h
9504	DBUS <= "10010101000000100"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- MVI R5 00000100
c582	DBUS <= "1100010110000010"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- STA R5 82h
9408	DBUS <= "1001010000001000"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- MVI R4 00001000
c483	DBUS <= "1100010010000011"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- STA R4 83h
9310	DBUS <= "1001001100010000"; wait for 10 ns; DBUS <= "ZZZZZZZZZZZZZZZZ"; wait for 40 ns;	--- MVI R3 00010000
c384	DBUS <= "1100001110000100";	--- STA R3 84h

	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
9220	DBUS <= "1001001000100000";	--- MVI R2 00100000
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
c285	DBUS <= "1100001010000101";	--- STA R2 85h
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
9140	DBUS <= "1001000101000000";	---MVI R1 01000000
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
c186	DBUS <= "1100000110000110";	--- STA R1 86h
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
90ff	DBUS <= "1001000011111111";	--- MVI R0 11111111
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
c087	DBUS <= "1100000010000111";	--- STA R0 87h
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	
	wait for 40 ns;	
11111111 + 10 0006	DBUS <= "0000000000000110";	--- ADD R0 R6
	wait for 10 ns;	
	DBUS <= "ZZZZZZZZZZZZZZZZ";	



```

        wait for 40 ns;

        DBUS <= "1100000010001000";          --- STA R0 88h
00000000 cy 1    c088
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "0000110000000101";          --- SUB R4 R5
0c05
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "1100010010001001";          --- STA R4 89h
00000100    1000-0100    c489
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "0001011000000100";          --- MOV R6 R4
1604
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "1100011010010000";          --- STA R6 90h
0100    c690
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "1101110110001001";          --- LDA R5 10001001
89h    r4    dd89
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 20 ns;
        DBUS <= "0000000011111111";
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 10 ns;

        DBUS <= "1100010110010001";          --- STA R5 91h
11111111    c591

```

```

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

c792    DBUS <= "1100011110010010";           --STA  R7 92h

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

8210    DBUS <= "1000001000010000";           -- JZ R2 00001000

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

9200    DBUS <= "1001001000000000";           -- MVI R2 00000000

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

        DBUS <= "1100001010010011";           --STA  R2 93h    c293
        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

8210    DBUS <= "1000001000010000";           -- JZ R2 00010000

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

8804    DBUS <= "1000100000000100";           -- JMP  00000100

        wait for 10 ns;
        DBUS <= "ZZZZZZZZZZZZZZZZ";
        wait for 40 ns;

-- insert stimulus here

wait;
end process;

```

END;